

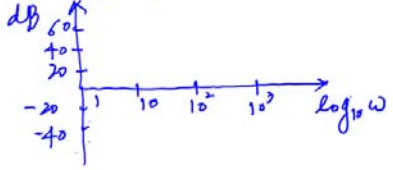


EE103 lect #16 Nov. 3, 2017
 HW 5 posted
 AZ 5 Nov. 6 (CM)

Bode plot

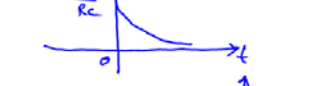


Textbook Example 5.2 (page 248-250)

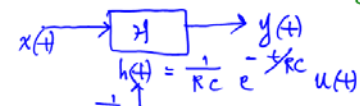

$x(t) = V u(t)$

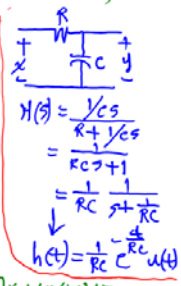$y(t) = h(t) * x(t) = \int_{-\infty}^{\infty} \frac{1}{Rc} e^{-\tau/Rc} u(\tau) \times V u(t-\tau) d\tau$
 $= V \int_0^t \frac{1}{Rc} e^{-\tau/Rc} d\tau = V (1 - e^{-t/Rc}) u(t)$



$X(\omega) = \mathcal{F}[x(t)] = V \mathcal{F}[u(t)] = V \left[\frac{1}{j\omega} + \pi \delta(\omega) \right]$

$H(\omega) = \int_{-\infty}^{\infty} \frac{1}{Rc} e^{-\tau/Rc} u(\tau) e^{-j\omega t} dt$
 $= \frac{1}{Rc} \int_0^{\infty} e^{-(\tau/Rc + j\omega)\tau} d\tau = \frac{1}{Rc} \left[\frac{e^{-(\tau/Rc + j\omega)\tau}}{-(\tau/Rc + j\omega)} \right]_0^{\infty}$
 $= \frac{1}{Rc} \left(0 + \frac{1}{\tau/Rc + j\omega} \right) = \frac{1}{1 + j\omega RC}$

$Y(\omega) = H(\omega) X(\omega) = \frac{1}{1 + j\omega RC} V \left[\frac{1}{j\omega} + \pi \delta(\omega) \right]$

$= V \left[\frac{1}{1 + j\omega RC} \frac{1}{j\omega} + \frac{1}{1 + j\omega RC} \pi \delta(\omega) \right]$
 $= V \left[\frac{-RC}{1 + j\omega RC} + \frac{1}{j\omega} + \pi \delta(\omega) \right]$
 $y(t) = V \left[-u(t) e^{-t/Rc} + u(t) \right] = V (1 - e^{-t/Rc}) u(t)$

Bode plot of $H(\omega)$
 section 5.4 pp. 245-248 (Textbook)

$x(t) \rightarrow H(\omega) \rightarrow Y(\omega)$ $H(\omega) = |H(\omega)| \angle H(\omega) = |H(\omega)| e^{j\angle H(\omega)}$



$H(\omega) = \frac{R}{j\omega L + \frac{1}{j\omega C} + R} = \frac{(j\omega C) R}{1 + (j\omega L)(j\omega C) + j\omega RC}$
 $= \frac{j\omega RC}{(1 - \omega^2 LC + j\omega RC)}$

In this circuit, at $\omega = 1/\sqrt{LC}$ $j\omega L + 1/j\omega C = 0$ (resonance) and $H(\omega) = 1$

$H(\omega) = |H(\omega)| \angle H(\omega) = |H(\omega)| e^{j\angle H(\omega)}$

$|H(\omega)| = \frac{|j\omega RC|}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$

(Case 1) $L = 1 \text{ mH}$, $C = 1 \mu\text{F}$, $R = 1 \text{ m}\Omega$

then $|H(\omega)| = \frac{\omega (10^{-3})(10^{-6})}{\sqrt{(1 - \omega^2 (10^{-3})(10^{-6}))^2 + (\omega (10^{-3})(10^{-6}))^2}}$
 $= \frac{\omega}{\sqrt{(1 - \omega^2 10^{-9})^2 + \omega^2}}$



- $\omega = 0$ $|H(\omega)| = 0$; $\omega = 1$, $H(1) = \frac{1}{\sqrt{(1 - 10^{-9})^2 + 1}}$
- $\omega = 10$ $|H(\omega)| = \frac{10}{\sqrt{(1 - 10^{-9})^2 + 10^2}} = 1$

$\omega = 10^2$ $|H(\omega)| = \frac{10^2}{\sqrt{(1 - (10^2)^2 10^{-9})^2 + (10^2)^2}} = 1$

$\omega = 10^3$ $|H(\omega)| = \frac{10^3}{\sqrt{(1 - (10^3)^2 10^{-9})^2 + (10^3)^2}} = 1$
 $\approx \frac{10^3}{10^3 \sqrt{2}} = \frac{1}{\sqrt{2}}$

$\omega = 10^4$ $|H(\omega)| = \frac{10^4}{\sqrt{(1 - (10^4)^2 10^{-9})^2 + (10^4)^2}} = \frac{10^4}{\sqrt{10^8 + 0.81}}$
 $= 1$

$\omega = 10^9$ $|H(\omega)| = \frac{10^9}{\sqrt{(1 - (10^9)^2 10^{-9})^2 + (10^9)^2}} = \frac{1}{\sqrt{2}}$

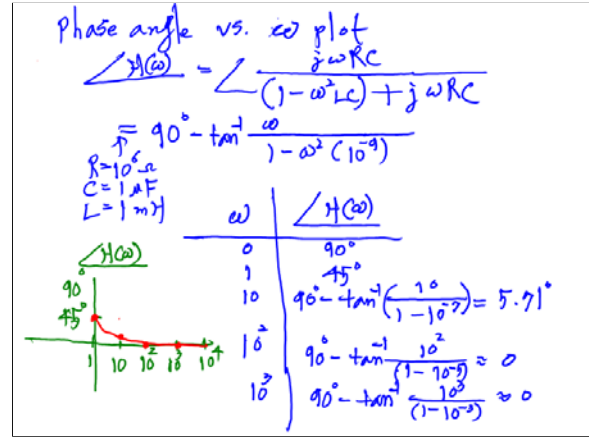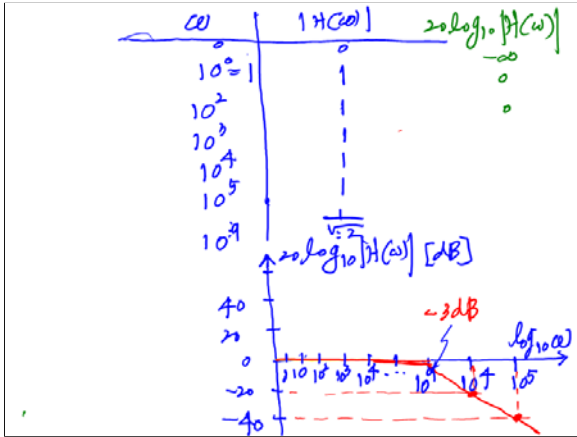

Example LC tank circuit

$v(t) = V \cos \omega t$
 $v(0) = V$ initial voltage across C

$$i_C = C \frac{dv}{dt} \quad v = L \frac{di_L}{dt} = L \frac{d(-i_C)}{dt}$$

$$= L \frac{d}{dt} \left[-C \frac{dv}{dt} \right] = -LC \frac{d^2 v}{dt^2}$$

$$LC \frac{d^2 v}{dt^2} + v = 0 \quad \text{if } v = V \cos \omega t$$

$$LC (-\omega^2 V \cos \omega t) + V \cos \omega t = 0 \Rightarrow LC \omega^2 = 1$$

$$\omega = \frac{1}{\sqrt{LC}} \text{ (resonant freq)} \quad v(t) = V \cos \frac{t}{\sqrt{LC}}$$

Parseval's Theorem

$$\int_{-\infty}^{\infty} |f(t)|^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(\omega)|^2 d\omega$$

Proof: $\int_{-\infty}^{\infty} |f(t)|^2 dt = \int_{-\infty}^{\infty} f(t) \overline{f(t)} dt = \int_{-\infty}^{\infty} f(t) \left(\frac{1}{2\pi} \int_{-\infty}^{\infty} \overline{F(\omega)} e^{j\omega t} d\omega \right) dt$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \overline{F(\omega)} \left(\int_{-\infty}^{\infty} f(t) e^{j\omega t} dt \right) d\omega = \frac{1}{2\pi} \int_{-\infty}^{\infty} \overline{F(\omega)} F(\omega) d\omega$$

For power signal $f(t)$,

$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} |f(t)|^2 dt < \infty$$

(examples) $\cos(t)$, $\sin(t)$, periodic signals
But their energy is infinite!

Truncated signal $f_T(t) = f(t) \text{rect}(t/T)$

$f_T(t) \leftrightarrow F_T(\omega)$

$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} |f_T(t)|^2 dt$$

$$\int_{-T/2}^{T/2} |f_T(t)|^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |F_T(\omega)|^2 d\omega$$

Parseval's Theorem

$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \left[\frac{1}{2\pi} \int_{-\infty}^{\infty} |F_T(\omega)|^2 d\omega \right]$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \lim_{T \rightarrow \infty} \frac{1}{T} |F_T(\omega)|^2 d\omega$$

$\beta_f(\omega)$ power spectral density

$$P = \frac{1}{2\pi} \int_{-\infty}^{\infty} \beta_f(\omega) d\omega$$

From the Fourier series of $f(t)$



$$f(t) = \sum_{k=-\infty}^{\infty} C_k e^{+jk\omega t}$$

$$F(\omega) = \frac{1}{2\pi} \sum_{k=-\infty}^{\infty} F(k\omega) \delta(\omega - k\omega)$$

Power $P = \sum_{k=-\infty}^{\infty} |C_k|^2 = C_0^2 + 2 \sum_{k=1}^{\infty} |C_k|^2$

$$= \frac{1}{4\pi^2} F(0) + \frac{1}{2\pi^2} \sum_{k=1}^{\infty} |F(k\omega)|^2$$

$\frac{1}{2\pi} F(k\omega) = C_k$

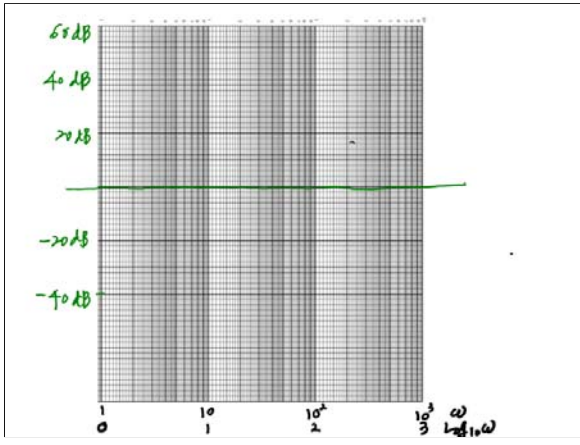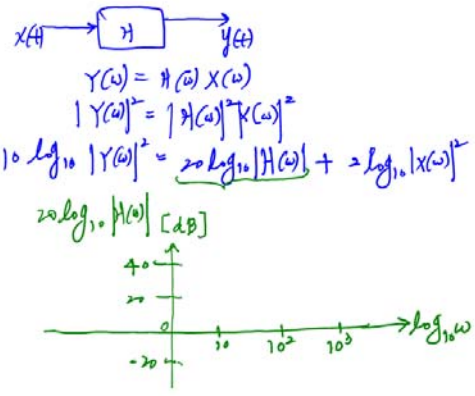


Block diagram: $\frac{10 \text{ m}\Omega}{\text{output}} \parallel \frac{0.1 \text{ }\mu\text{F}}{\text{input}}$

$$H(\omega) = \frac{R}{j\omega C + R} = \frac{1}{1 + j\omega RC}$$

For $R=1$, $H(\omega) = \frac{1}{1 + j\omega(10^2 \cdot 10^{-7})} = \frac{1}{1 + j\omega}$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$

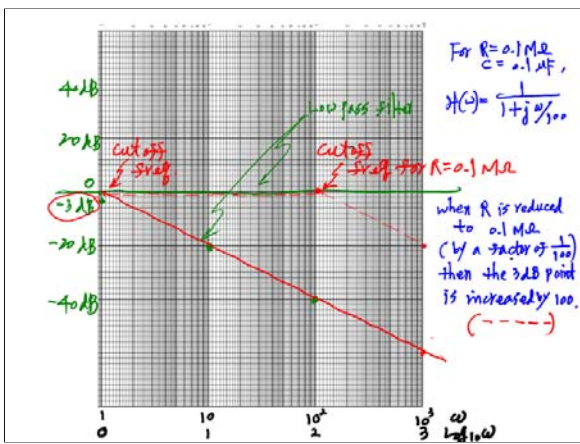- $\omega = 1$: $\frac{1}{\sqrt{2}}$, $20 \log_{10} \frac{1}{\sqrt{2}} = -10 \log_{10} 2 = -3 \text{ dB}$
- $\omega = 10$: $\frac{1}{10}$, $20 \log_{10} \frac{1}{10} = -20 \text{ dB}$
- $\omega = 10^2$: $\frac{1}{10^2}$, $20 \log_{10} \frac{1}{10^2} = -40 \text{ dB}$



In general

$$H(\omega) = K \frac{(1 + \frac{\omega}{\omega_{z1}})(1 + \frac{\omega}{\omega_{z2}}) \dots (1 + \frac{\omega}{\omega_{zn}})}{(1 + \frac{\omega}{\omega_{p1}})(1 + \frac{\omega}{\omega_{p2}}) \dots (1 + \frac{\omega}{\omega_{pn}})}$$

$$20 \log_{10} |H(\omega)| = 20 \log_{10} |K| + \sum_{j=1}^m 20 \log_{10} |1 + \frac{\omega}{\omega_{zj}}| - \sum_{k=1}^n 20 \log_{10} |1 + \frac{\omega}{\omega_{pk}}|$$

Example

$$H(\omega) = 100 \frac{(1 + \frac{\omega}{100})}{(1 + \frac{\omega}{10})(1 + \frac{\omega}{1000})}$$

$$20 \log_{10} |H(\omega)| = 20 \log_{10} 100 + 20 \log_{10} |1 + \frac{\omega}{100}| - 20 \log_{10} |1 + \frac{\omega}{10}| - 20 \log_{10} |1 + \frac{\omega}{1000}|$$

