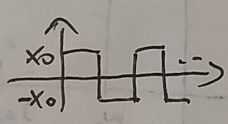



(a) ①

- (1) The V_p is a square wave.
- (2) From 4.3, it is given for even K F.S coefficients = 0 for odd K $C_K = \frac{-j2X_0}{\pi K}$, where $X_0 = 10$.
- (3) Hence the first three non-zero harmonics are as follows
 $C_1 = \frac{-20j}{\pi}$, $C_3 = \frac{-20j}{3\pi}$, $C_5 = \frac{-20j}{5\pi}$, $C_{-1} = \frac{20j}{\pi}$, $C_{-3} = \frac{20j}{3\pi}$, $C_{-5} = \frac{20j}{5\pi}$
- (4) Calculate system Transfer function. This will help us evaluate corresponding system coefficients.
- (5) Multiply V_p & system coefficients to get o/p coefficients

input = square wave.



where $X_0 = 10V$

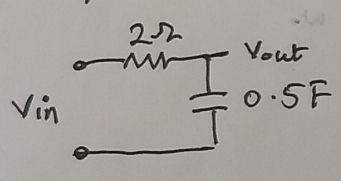

$$V_{in} = \frac{Z_c}{Z_c + R} \times V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{Z_c}{Z_c + R}$$

$$Z_c = \frac{1}{j\omega C}$$

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{1/j\omega C}{1/j\omega C + R}$$

$$= \frac{1/j\omega C}{1 + j\omega RC}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$R = 2\Omega, C = \frac{1}{2}F$$

$$\Rightarrow H(j\omega) = \frac{1}{1 + j\omega}$$

∴ The system coefficients are:

$$H(j1) = \frac{1}{1+j}, \quad H(j3) = \frac{1}{1+3j}, \quad H(j5) = \frac{1}{1+5j}$$

$$= \frac{1-j}{2}, \quad = \frac{1-3j}{10}, \quad = \frac{1-5j}{26}$$

For o/p coefficient

$$H(-j) = \frac{1+j}{2}, \quad H(-j3) = \frac{1+3j}{10}, \quad H(-j5) = \frac{1+5j}{26}$$

$$\omega_0 = \frac{2\pi}{T_0}, \quad T_0 = 2\pi$$

$$= \frac{2\pi}{2\pi} = 1 \text{ rad/s.}$$

$$C_1 = C_{in1} \times H(j\omega_0)$$

$$= \frac{-20j}{\pi} \cdot \frac{1-j}{2}$$

$$= \frac{-10}{\pi} (1+j) \Rightarrow 4.50 \angle -135^\circ$$

$$C_3 = \frac{-20j}{3\pi} \cdot \frac{1-3j}{10}$$

$$= \frac{-2}{3\pi} (1+3j)$$

$$\Rightarrow 0.67 \angle -108^\circ$$

$$C_5 = \frac{-20j}{5\pi} \cdot \frac{1-5j}{26}$$

$$= \frac{-2}{13\pi} (1+5j)$$

$$\Rightarrow 0.25 \angle -101^\circ$$


$$C_{-1} = \frac{20j}{\pi} \times \frac{(1+j)}{2}$$

$$= \frac{10}{\pi} (-1+j) = \frac{-10}{\pi} (1-j) = 4.5 \angle 135^\circ$$


$$C_{-3} = \frac{-2}{3\pi} (1-3j) = 0.67 \angle 108^\circ$$

$$C_{-5} = \frac{-2}{13\pi} (1-5j) = 0.25 \angle 101^\circ$$

Amp Response.

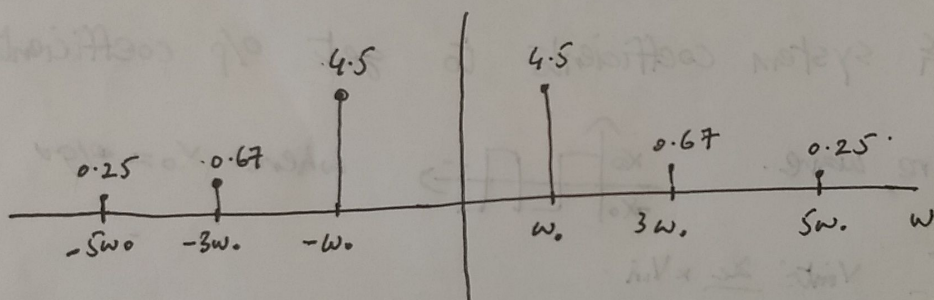

Phase Response.

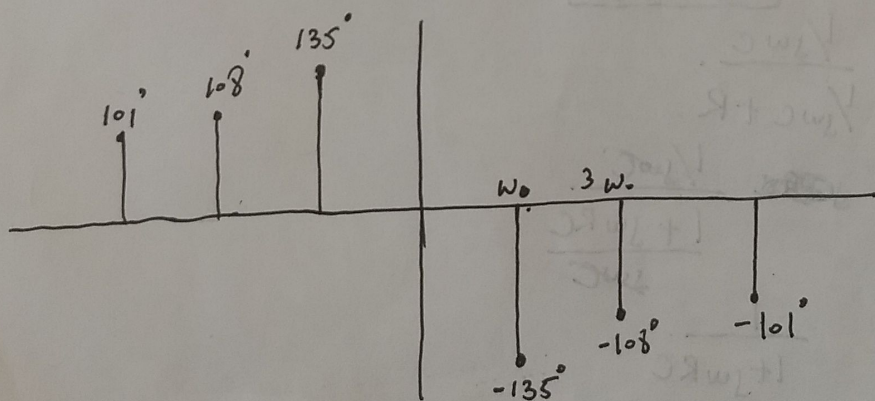

$$w_0 = \frac{2\pi}{T}, T = 2\pi$$

$$= 1 \text{ rad/s}$$

$$H(w) = \frac{1}{1+jw}$$

(c) periodic function $x(t)$ is represented as.

$$x(t) = A_0 + \sum_{k=1}^{\infty} C_k e^{j\omega_k t}$$

The DC value will have no effect on the first 3 harmonics. They remain the same as in part 1.

As for the DC component


$$C_0 = H(0) C_{in0}$$

$$= 20V.$$

$$C_{in0} = 20V.$$

$$H(j\omega) = \frac{1}{1+j\omega}$$

$$H(0) = 1$$

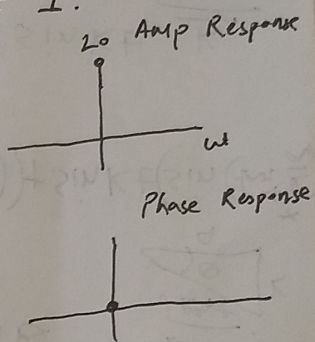

(d) There are multiple ways to ans this.

$$H(j\omega) = \frac{1}{1+j\omega}$$

For $\omega \gg 1$.

$$1+j\omega \approx j\omega.$$

$$\therefore H(j\omega) \approx \frac{1}{j\omega}$$

For higher values of 'w' $H(j\omega) \rightarrow 0$

For $\omega \ll 1$.

$$1+j\omega \approx 1.$$

$$H(j\omega) = 1$$

Hence a Low pass filter.



(e) The fundamental frequency has changed from 1rad/s \rightarrow 2rad/s
 this will change the distance between the harmonics

(2) $\frac{1}{p}$ signal

$$x(t) = \sum_{k=1}^{\infty} \cos(kt)$$

Impulse Response of system.

$$h(t) = e^{-at} u(t)$$

From Table 4.5, steady state sinusoidal response for LTI system with $\frac{1}{p}$ $x(t) = X \cos(\omega t + \phi)$

$$|X| |H(j\omega)| \cos(\omega t + \phi + \angle H(j\omega)) \quad \text{--- 4.41}$$

Here $X = 1$ $\omega = K$
 $\phi = 0$.

$$\begin{aligned} H(j\omega) &= \int_{-\infty}^{\infty} h(t) e^{-j\omega t} dt \\ &= \int_{-\infty}^{\infty} e^{-at} u(t) e^{-j\omega t} dt \\ &= \int_{-\infty}^0 e^{t(a+j\omega)} u(t) dt + \int_0^{\infty} e^{-t(a+j\omega)} u(t) dt \\ &= \int_0^{\infty} e^{-t(a+j\omega)} dt \end{aligned}$$

$$H(j\omega) = \frac{1}{j\omega + a}$$

According to 4.41. And $x=1, \omega=k, t=0$

$$Y(t) = \sum_{k=1}^{\infty} |H(jk)| \cos(kt + \angle H(jk))$$

For $H(jk) = \frac{1}{jk\tau a}$

$$|H(jk)| = \frac{1}{\sqrt{k^2 + a^2}}$$

$$\angle H(jk) = \tan^{-1}\left(-\frac{k}{a}\right)$$

$$Y(t) = \sum_{k=1}^{\infty} \frac{1}{\sqrt{k^2 + a^2}} \cos\left(kt + \tan^{-1}\left(-\frac{k}{a}\right)\right)$$

$$= \sum_{k=1}^{\infty} \frac{1}{\sqrt{k^2 + a^2}} \cos\left(kt - \tan^{-1}\left(\frac{k}{a}\right)\right)$$

$$\Rightarrow \cos(A \mp B) = \cos A \cos B \pm \sin A \sin B$$

$$= \sum_{k=1}^{\infty} \frac{1}{\sqrt{k^2 + a^2}} \cos kt \cos\left(\tan^{-1}\left(\frac{k}{a}\right)\right) + \sin kt \sin\left(\tan^{-1}\left(\frac{k}{a}\right)\right)$$

$$= \sum_{k=1}^{\infty} \frac{1}{\sqrt{k^2 + a^2}} \cos kt \frac{a}{\sqrt{a^2 + k^2}} + \sin kt \frac{k}{\sqrt{a^2 + k^2}}$$

$$Y(t) = \sum_{k=1}^{\infty} \frac{a \cos(kt) + k \sin(kt)}{a^2 + k^2}$$

